

# Lab 2: OpAmps

---

Mark and Jim

## Q1

Figure: Q1 Schematic

**With  $V_{in} = 0$  (input tied to ground), measure and record the DC output voltage with a DMM. What voltage do you expect, and what do you measure? Can you explain?**  $V_o = -575\text{nV}$ . In the ideal case, its expected to be a  $V_o = 0\text{V}$ . However, the nonideal input offset voltage of a real world op amp leads to a drift in the output voltage at equilibrium.

**Provide a 0.10 Vpp 10KHz sinewave input. Measure and record the gain of the amplifier and explain why the gain does not equal 100.**

$$V_{\text{pkpk, in}} = 64\text{mV}$$

$$V_{\text{pkpk, out}} = 551\text{mV}$$

The gain doesn't equal 100 because the input resistance was designed to be  $1\text{k}\Omega$ , so the signal is being significantly attenuated.

**With a 0.10 Vpp 1KHz sinewave input, slowly increase the input voltage as you observe the amplifier output waveform; look for saturation. Measure and record the maximum positive and negative voltage swings:**

Bottom rail saturation:

Output = -11.1V

Input = 1.0V

Top rail saturation:

Output = 12.7V

Input = -1.8V

**\*\*Why is output voltage swing important? \*\*** Output voltage swing determines the absolute min/max of your input signal, defining the usable range for a given gain.