Part 3 Part 1 Q101 Q302 NPN R103 150R R304 150R R101 R303 C301 100uF C101 R306 5R6 R105 5R6 100uF R102 R104 470R R305 470R R301 10K ▲ D101 6.2V GND GND GND Q301 R302 GND GND GND ALL BJTs TIP31C UNLESS OTHERWISE NOTED Drawn by: Mark Vaughn ZAM Industries, LLC Sheet: / File: Lab07.kicad\_sch Title: Linear Power Supplies Date: 2024-03-02 Size: A5 Rev: 0 KiCad E.D.A. kicad 7.0.5 ld: 1/1